
# Chapter 18
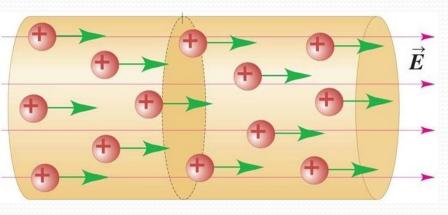
#### Current

= motion of charge
 a steady flow of charge → a steady force on mobile charges




$$I = \frac{\Delta Q}{\Delta t}$$

current = amount of charge moving through given cross section per unit time

$$[I]$$
 = ampere,  $1 A = 1 C / s$ 
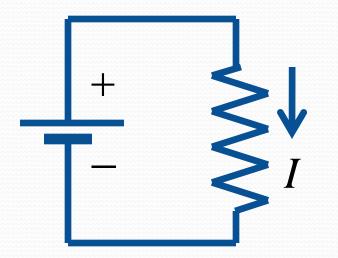
### Current in a Complete Circuit

- current is the same at all cross sections, it does not emerge from the positive battery terminal and disappear in the negative terminal
- speed to establish current >> electron drift speed



conventional current flow: from + to - (opposite to electron motion)

## Resistance and Resistivity

Electric field is proportional to the potential difference between the ends of a conductor, and current is caused by electric field

$$R = \frac{V}{I}$$

Ohm's law: For many materials, current is proportional to potential difference (voltage)


**Resistance**: the proportionality factor

Resistance is for an object, resistivity for material

Resistivity ρ: geometry independent

$$R = \rho \frac{L}{A}$$

### Temperature Dependence of R

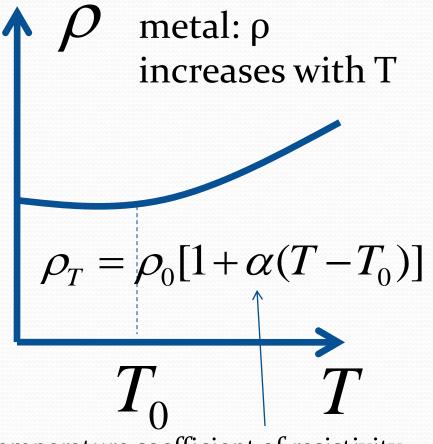

superconductor: ρ drops to zero below  $T_{C}$ used in superconducting magnets at the LHC

temperature coefficient of resistivity

#### **Energy and Power in Circuits**

 as charge passes through a circuit, the electric field does work on the charge

$$\Delta W = V \Delta Q$$
 — definition of potential difference

$$\Delta Q = I\Delta t$$
 — definition of current

$$VI = \frac{\Delta W}{\Delta t} = P$$

power = work/unit time

from Ohm's law:

$$P = I^2 R = \frac{V^2}{R}$$

#### **Alternating Current**

- Direct current: charges move steadily in one direction
- Alternating current: the direction changes over time

$$V = V_0 \sin \omega t$$

$$I = \frac{V}{R} = \frac{V_0}{R} \sin \omega t = I_0 \sin \omega t$$

#### **Alternating Current Power**

Power is always positive, can talk about average power

$$P = I^{2}R = I_{0}^{2} \sin^{2} \omega t \qquad I_{\text{rms}} = I_{0} / \sqrt{2}$$

$$-\frac{1}{2}I_{0}^{2}R = \frac{1}{2}\frac{V_{0}^{2}}{R} \qquad \frac{V_{\text{rms}} = V_{0} / \sqrt{2}}{P = I_{\text{rms}}V_{\text{rms}}}$$