


# Chapter 19

## DC Circuits
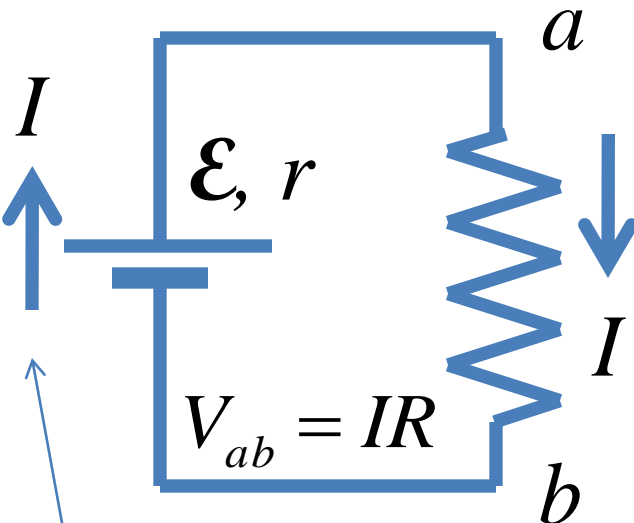
# Electromotive Force

= the influence that moves charge from lower to higher potential (against electric field)

emf is not a force ☺ It's energy per charge – like potential  
 emf origin: chemical (battery), magnetic field (generator),...



ideal emf source:  $V_{ab} = \mathcal{E}$   
 real emf source:  $V_{ab} = \mathcal{E} - Ir$


terminal voltage  
 internal resistance

$$I = \frac{\mathcal{E}}{R + r}$$

current through resistance:  
 due to potential difference

current inside the battery:  
 from - to + due to emf

# Resistors in Series

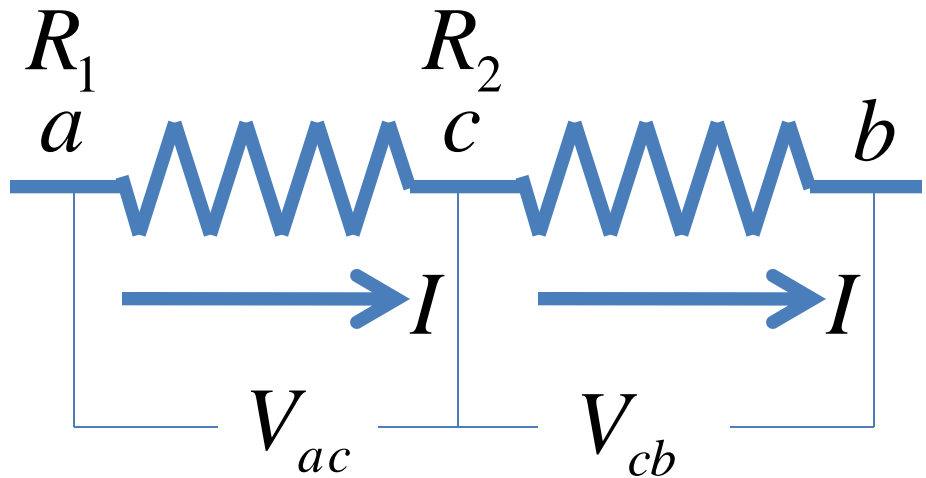

$$V_{ac} = IR_1$$

$$V_{cb} = IR_2$$

$$V_{ab} = IR_{eq}$$

current is the same, potential difference adds up  
(no charge accumulation)

$$V_{ab} = V_{ac} + V_{cb}$$

more than two resistors in series:

$$R_{eq} = R_1 + R_2$$


$$R_{eq} = R_1 + R_2 + \dots + R_n$$

# Resistors in Parallel

$$V_{ab} = I_1 R_1$$

$$V_{ab} = I_2 R_2$$

$$V_{ab} = I R_{eq}$$

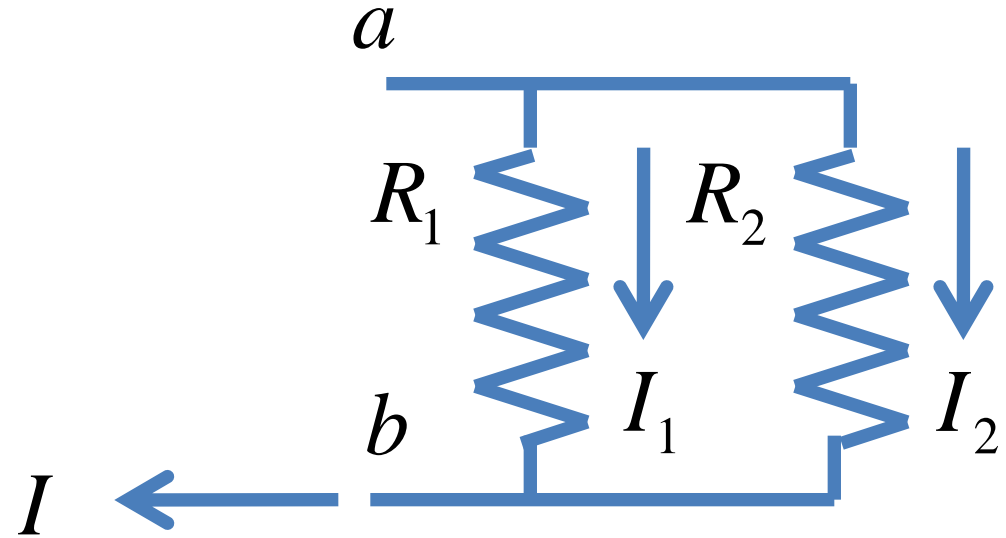

potential difference is the same, current adds up  
(no charge accumulation)

$$I = I_1 + I_2$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

more than two resistors in parallel:

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

# Kirchhoff's Rules





- use them when the circuit can't be reduced to series/parallel combinations

**Point rule:** algebraic sum of all currents into a point is 0


**Loop rule:** algebraic sum of all potential differences in a loop is 0

- label currents
- for each junction, write down the sum of currents
- for each loop, write down the sum of potential differences

# Rules for Loops

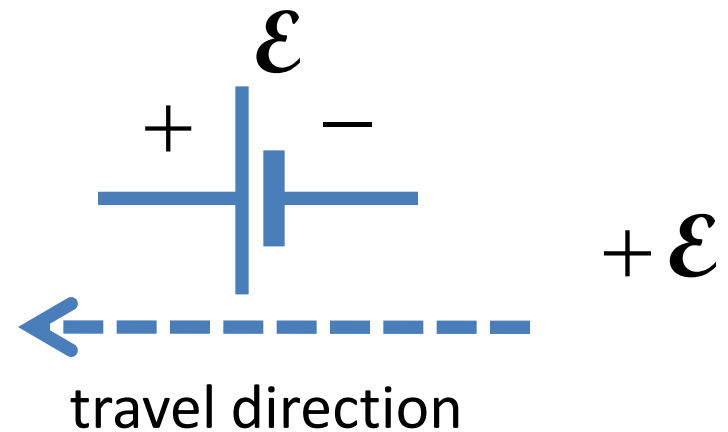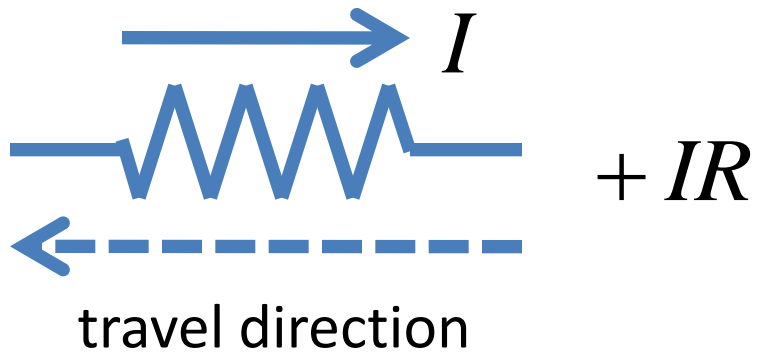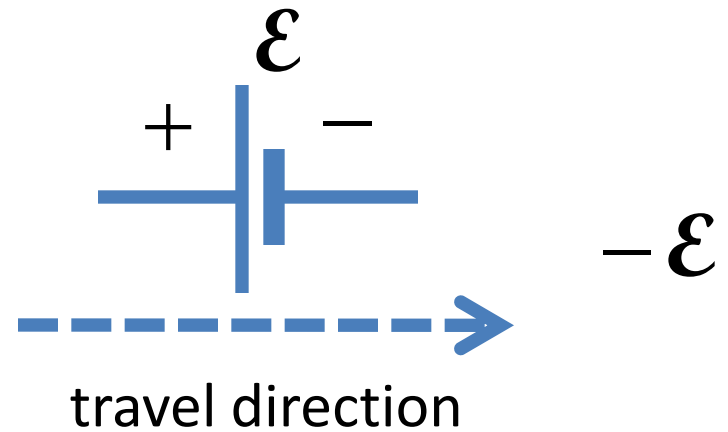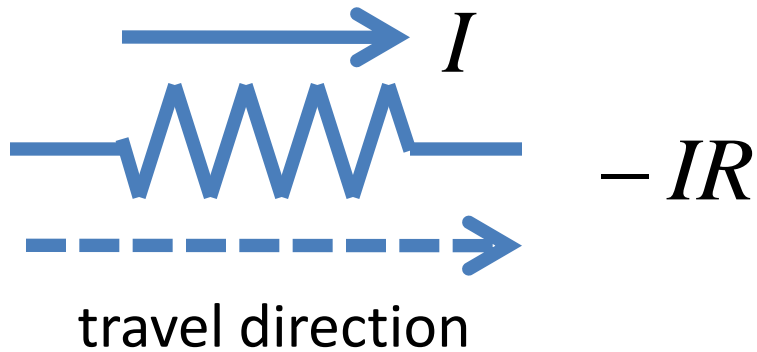

# Capacitors in Parallel

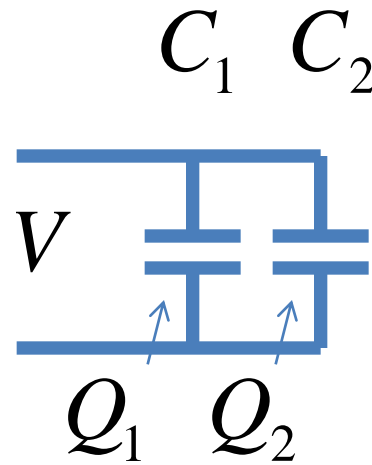

$$Q_1 = C_1 V$$


$$Q_2 = C_2 V$$

voltage on both capacitors is the same!


$$Q = Q_1 + Q_2 = V(C_1 + C_2)$$

$$C_{eq} = \frac{Q}{V}$$

# Capacitors in Parallel: formula

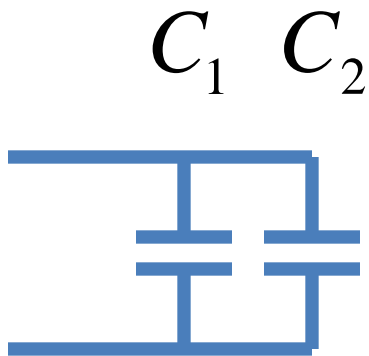


$$C_{eq} = C_1 + C_2$$

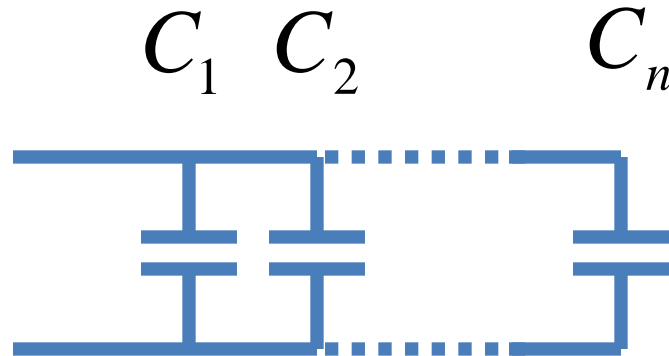

$$C_{eq} = C_1 + C_2 + \dots + C_n$$



# Capacitors in Series

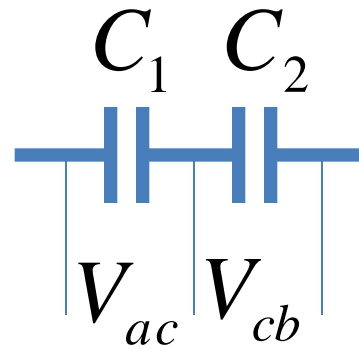

$$V_{ac} = \frac{Q}{C_1}$$

$$V_{cb} = \frac{Q}{C_2}$$


charge on both capacitors is the same! (conservation of charge)

$$V_{ab} = V_{ac} + V_{cb} = Q \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \quad C_{eq} = \frac{Q}{V_{ab}}$$
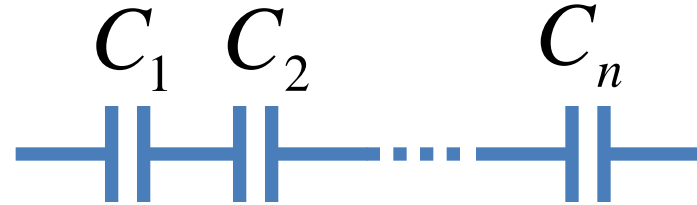
# Capacitors in Series: formula



$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$



$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}}$$


# Resistance-Capacitance Circuits

Switch open

$$I = 0$$

$$V_{ab} = V_{bc} = 0$$

$$Q = 0$$

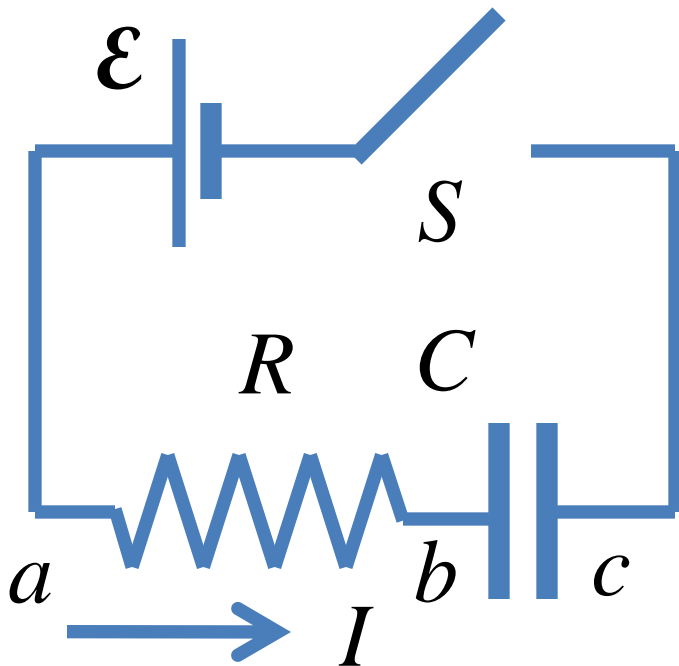

# Resistance-Capacitance Circuits


Switch closed ( $t = 0$ )

$Q = 0$  C needs time to charge

$$V_{bc} = \frac{Q}{C} = 0$$

$$V_{ab} = IR \neq 0$$
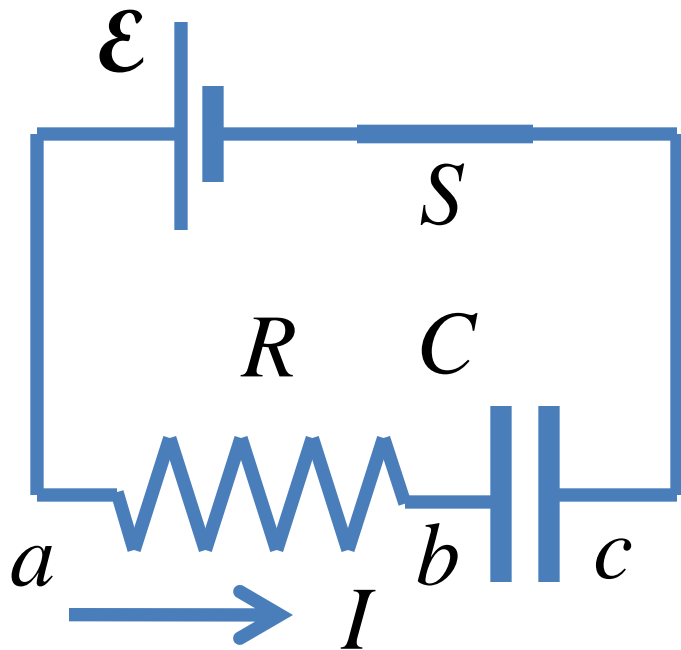
$$\mathcal{E} = IR \quad \text{Kirchhoff's rule}$$




# Resistance-Capacitance Circuits

Switch closed ( $t > 0$ )

$$Q > 0$$


$$V_{bc} = \frac{Q}{C} > 0$$
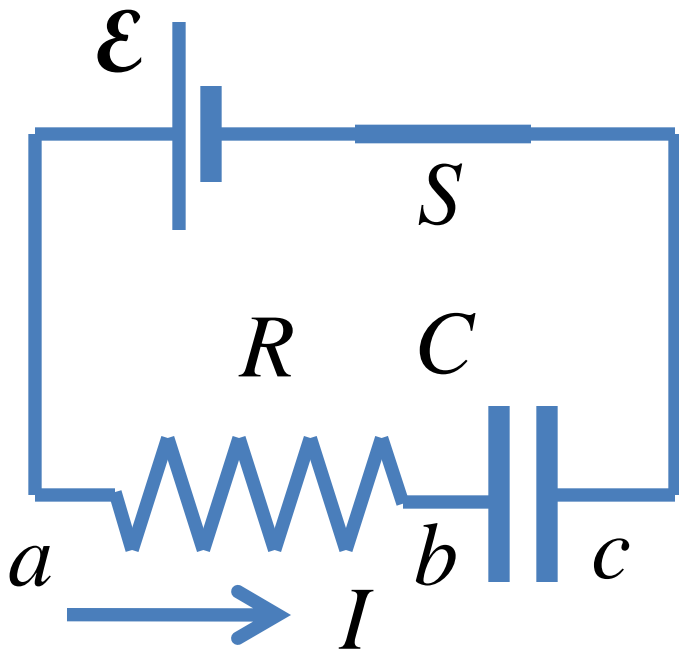
$$\mathcal{E} = IR + \frac{Q}{C} \quad (I < I_0)$$



# Resistance-Capacitance Circuits

Switch closed ( $t = \infty$ )

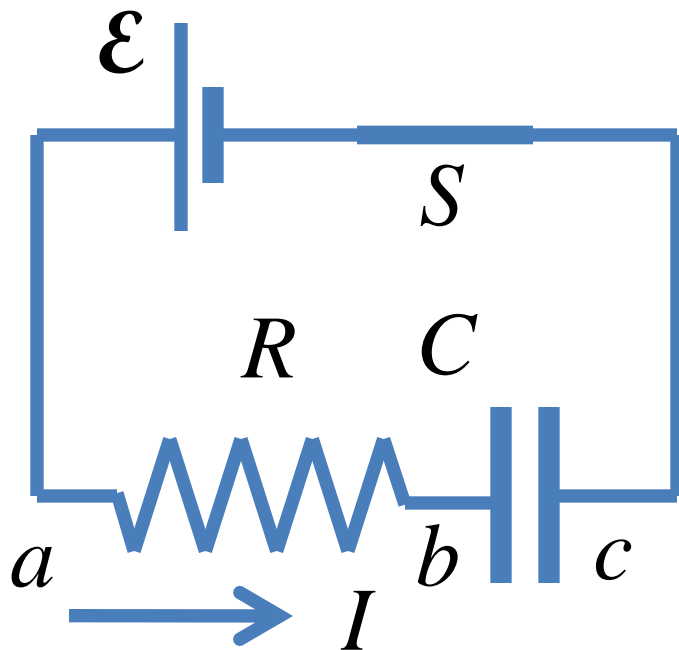

$$I = 0$$

no current in static condition (C plates insulated!)

$$V_{ab} = 0$$

$$\mathcal{E} = \frac{Q}{C}$$



final charge doesn't depend on R

# Current and Charge vs time

$$\mathcal{E} = IR + \frac{Q}{C} \quad \text{where} \quad I = \frac{\Delta Q}{\Delta t} \quad \text{-- need calculus to solve it}$$


$$\text{Answer: } I = I_0 e^{-t/RC}, \quad Q = Q_{final} (1 - e^{-t/RC})$$

$$e = 2.71828\dots$$

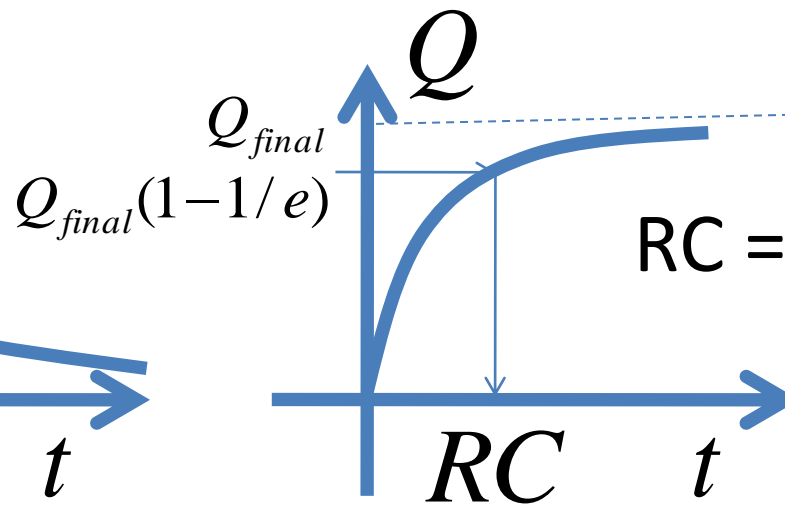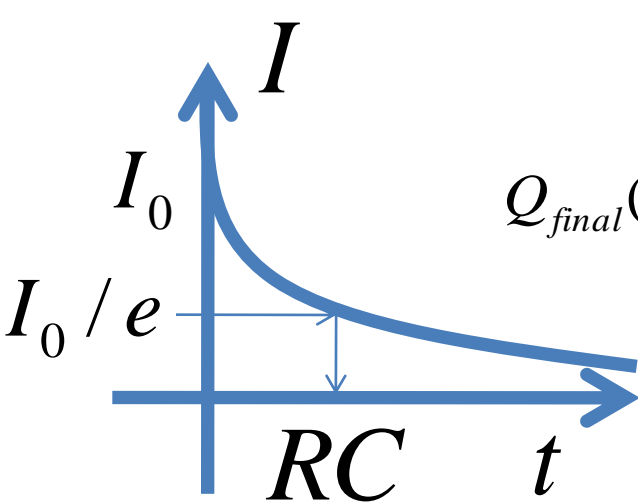

$RC = \text{relaxation time}$

# Capacitor Discharge

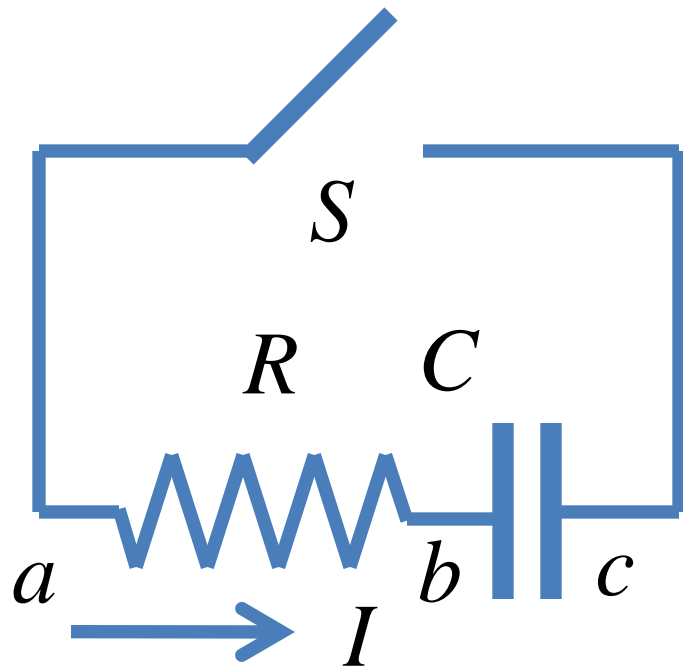

$$t = 0$$

$$Q = CV_0$$

$$I = -\frac{V_{bc}}{R}$$

$$I = I_0 e^{-t/RC}, Q = Q_0 e^{-t/RC}$$

