


Physics 1214, Homework #3 (due 9/12)

M1 Two identical metal rods are welded together end to end. If each rod has a length  $L$  and resistivity  $\rho$ , the resistivity of the combination will be

- A.  $4\rho$ .
- B.  $2\rho$ .
- C.  $\rho$ .
- D.  $\rho/2$ .

M2 Consider the circuit made of a  $R = 100 \Omega$  resistor, voltage source  $V$ , and fuse  $F$ . The fuse breaks if the instantaneous current in the circuit reaches 1 A. Which of the following voltage sources can be used in the circuit without breaking the fuse? Mark all possible choices.

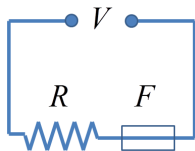- A. 120 V direct current.
- B. 80 V direct current.
- C. 120 V alternating current (standard U.S. line).
- D. 80 V alternating current.



## Problems

- P1 A potential difference of 10 V is applied to a copper wire of radius  $r = 0.5$  mm and length  $L = 1$  m. Find the power dissipated in the wire. The copper resistivity  $\rho = 1.68 \times 10^{-8}$   $\Omega\cdot\text{m}$ .
- P2 The peak value of an alternating current in a 1500 W device is 3 A. What is the rms voltage across it?
- P3 At \$0.12/kWh, what does it cost to leave a 25 W porch light on day and night for a year?
- P4 A heater coil connected to a standard 120 V<sub>rms</sub> ac line has a resistance of 36  $\Omega$ . What is the average power used?